

# EE228 – HW3 Report Track & Hold Circuits

Muhammad Aldacher  
Student ID: 011510317


# Overview

1. S/H using Ideal switch
2. S/H using NMOS or PMOS
3. S/H using CMOS Transmission Gate (TG)
4. Bootstrapped Circuits
  - a) Using Ideal Switches
  - b) Using transistors [2 topologies]
5. Summary

(1)

S/H Using Ideal Switch

# Circuit

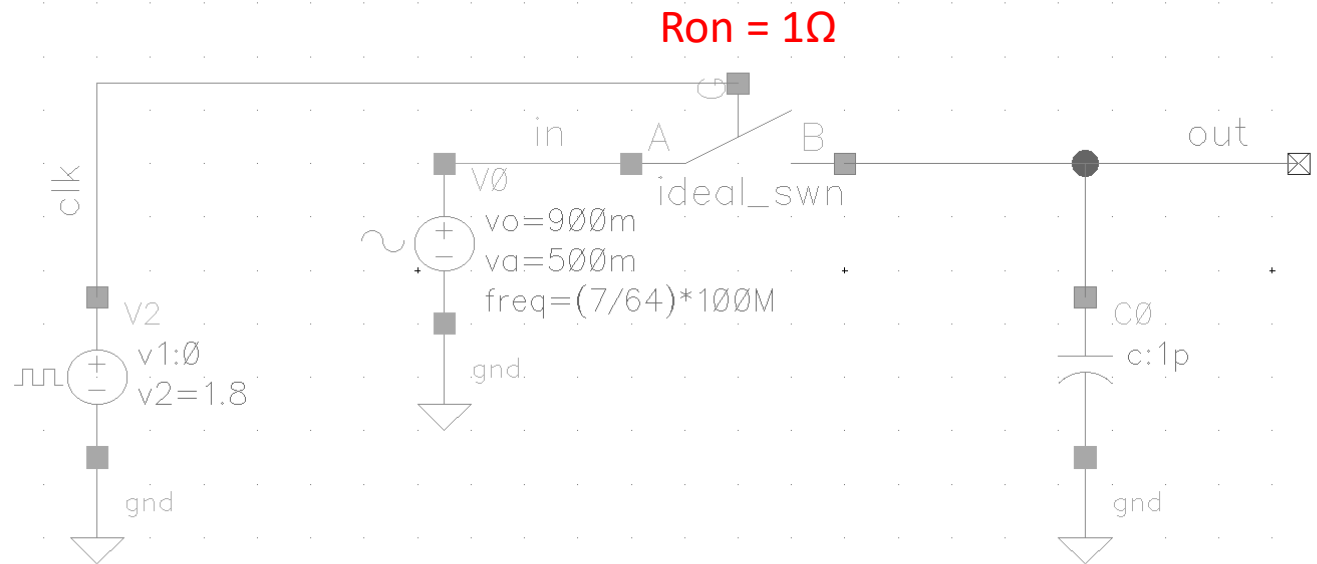

- Increasing the  $R_{on}$  of the switch, increases  $\tau = RC$  ...  
This decreases ENOB, SINAD, SNR, & SFDR.

# Waveforms


Sun Mar 4 12:08:28 2018

Transient Response

Name Vg


■ /in

Input  
Signal

 


■ /clk

Clock

 


■ /out

output  
of S/H

 

 
# DFT


db20(dft(v("/out" ?result "tran") 9n 649.0n 64 "Rectangular"))



# DFT (MATLAB)

 

# Using PrettyFFT function


 




(2)

S/H Using NMOS or PMOS



# Circuit

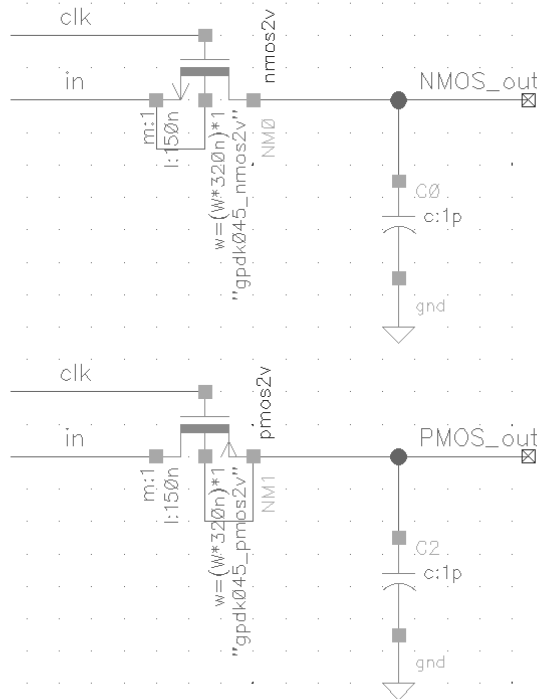 
 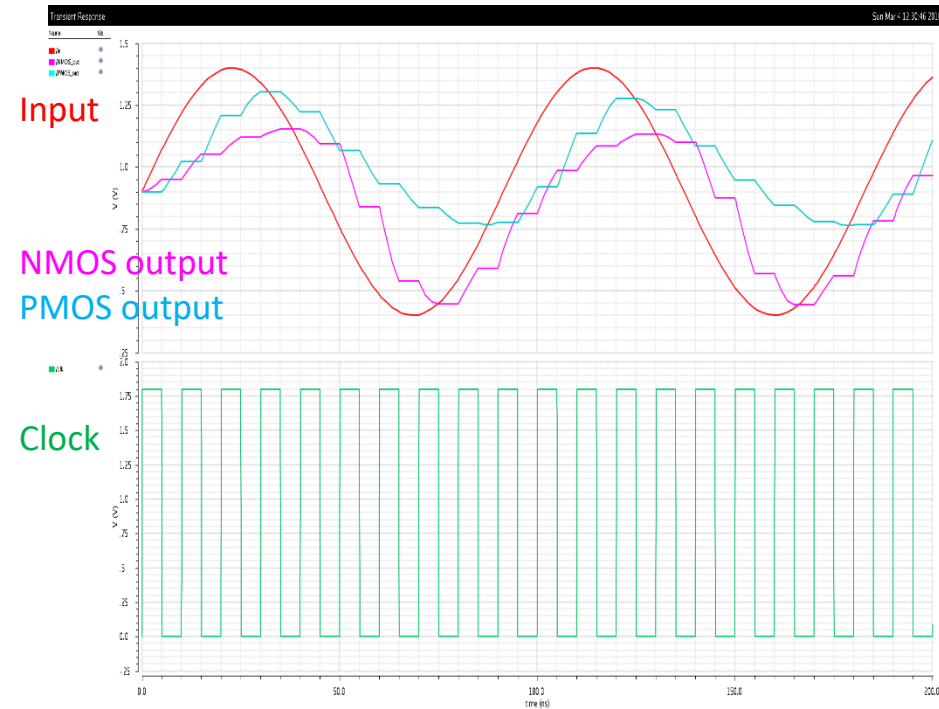
# Waveforms

$$\text{Lower } \left(\frac{W}{L}\right)_{n,p}$$

$$\text{Higher } \left(\frac{W}{L}\right)_{n,p}$$



- NMOS is better for passing smaller  $V_{in}$ , while PMOS is better for passing larger  $V_{in}$ .
- Increasing  $(W/L)$ , decreases  $R_{on}$  of the transistor, improving the S/H circuit performance.

# Waveforms

$$At \left( \frac{W}{L} \right)_{n,p} = 34 \times \left( \frac{320nm}{150nm} \right)$$

Maximum Allowed size  
for this technology

Thu Mar 8 00:06:18 2018

Transient Response

Name Vb

■ /in

Input  
Signal

■ /clk


Clock

■ /NMOS\_out


NMOS  
output

■ /PMOS\_out


PMOS  
output

 


# DFT of NMOS output

 

# DFT of NMOS output (MATLAB)

 

# Using PrettyFFT function

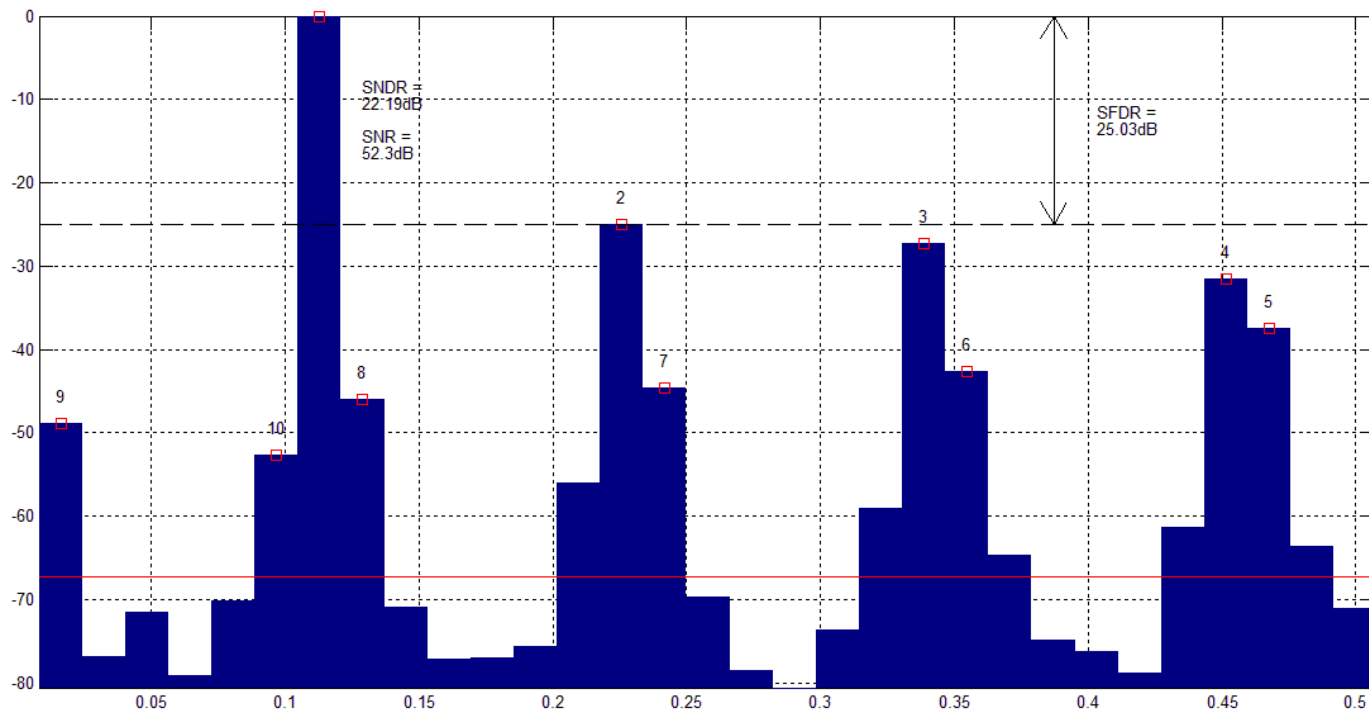


# DFT of PMOS output

db20(dft(v("/PMOS\_out" ?result "tran" 4n 644.0n 64 "Rectangular"))

Name

spectrum\_PMOS\_out  
spectrum\_PMOS\_out

DFT of  
PMOS  
output

 


Measurement Value


PMOS_out	
ENOB	3.4432156 (bits)
SINAD	22.491158 (dB)
SNR	22.491158 (dB)
SFDR	25.345154 (dB)
THD	0 (%)
Signal ...	-6.4715296 (dB)
DC Po...	-0.67037236 (dB)
Noise F...	-44.014188 (dB)
Noise F...	-105.81451 (dB)



# DFT of PMOS output (MATLAB)

 


# Using PrettyFFT function

 

(3)

S/H Using CMOS Transmission Gate

# Circuit

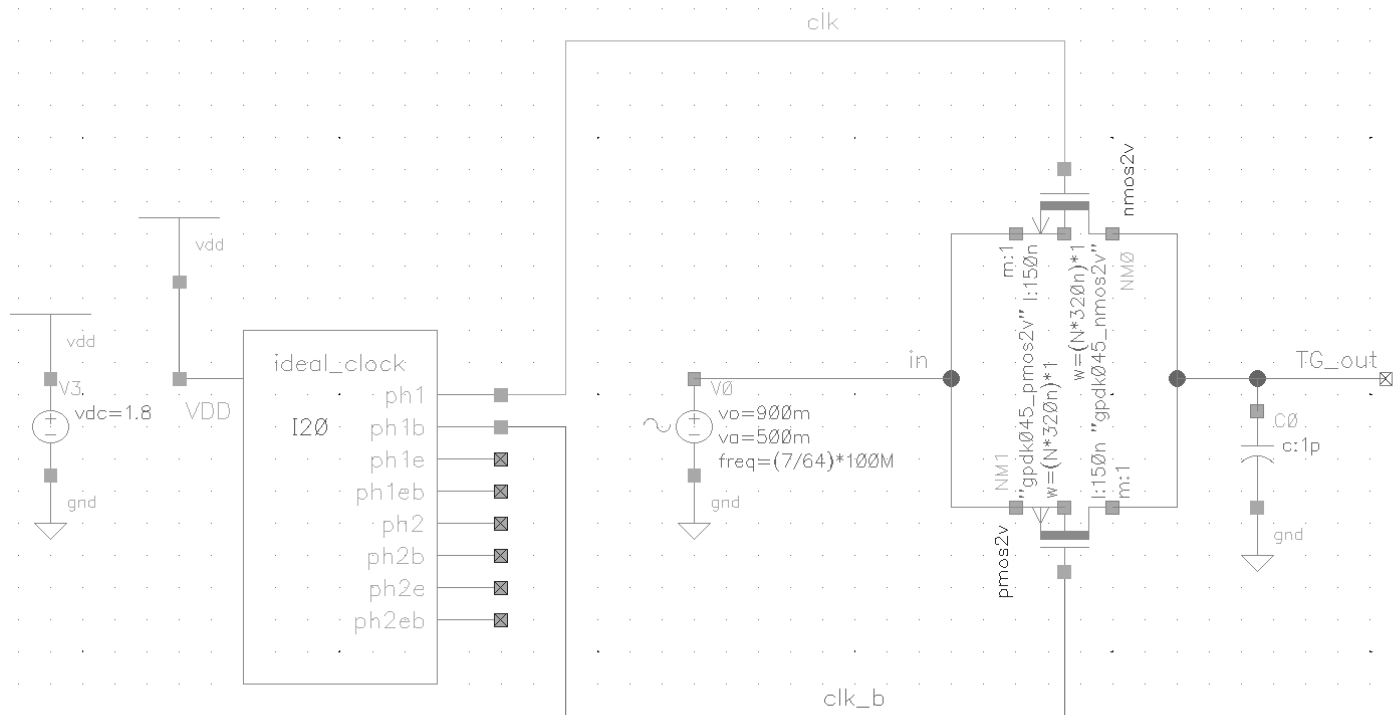

# Waveforms

$$At \left( \frac{W}{L} \right)_{n,p} = 34 \times \left( \frac{320nm}{150nm} \right)$$

Max size for best  
ENOB & performance

Sun Mar 4 14:14:17 2018

Transient Response

Name Vg

■ /in


Input  
Signal

■ /clk

Clock


■ /TG\_out

output  
of S/H

 

 
# DFT of TG output


dbz20(dft(v("TG\_out" ?result "tran") 9n 649.0n 64 "Rectangular"))



# DFT of TG output (MATLAB)

 

# Using PrettyFFT function

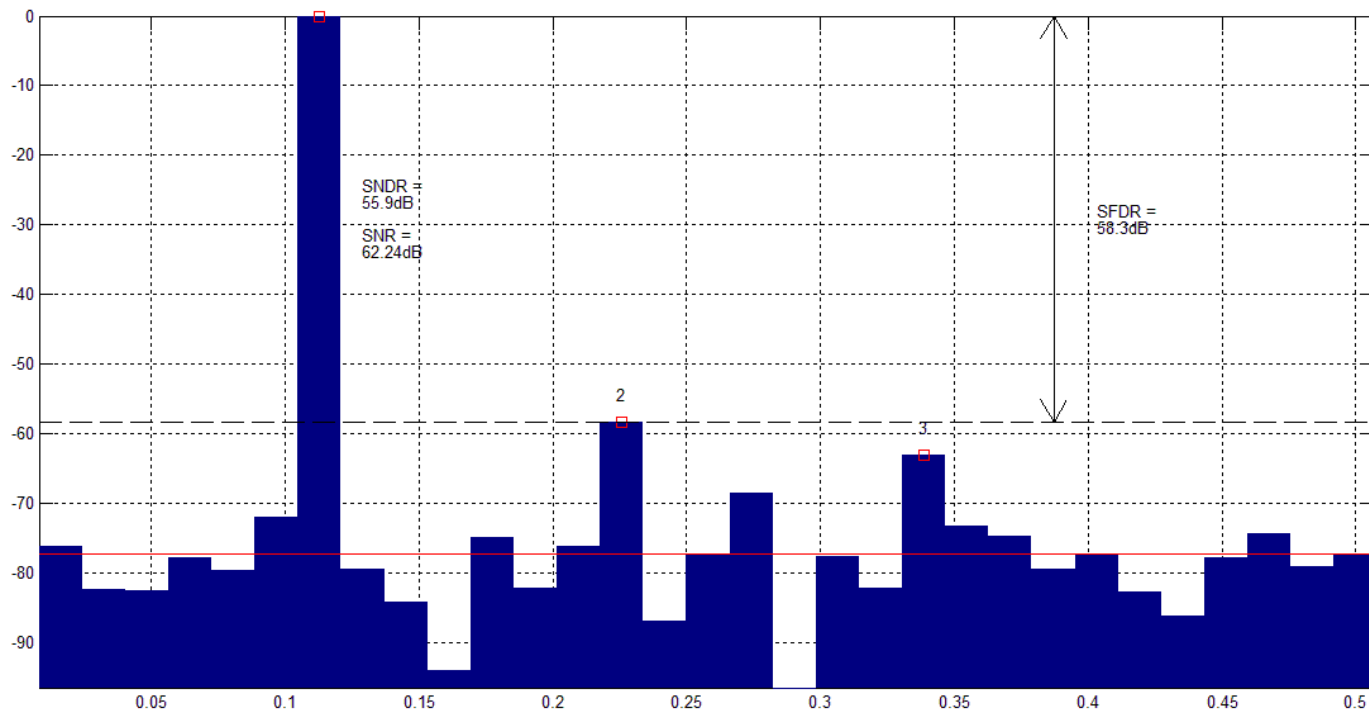



# DFT of TG output


- Notes:
  - The TG gives better performance than NMOS only or PMOS only, at the same (W/L).
  - Increasing  $(W/L)_{n,p}$  , decreases  $R_{on}$  of the TG, improving the S/H circuit performance.
  - With the maximum size for both transistors in the TG (best performance), the Maximum ENOB achieved = 9.29 bits (<10 bits).
  - Tradeoff:
    - ➔ Increasing  $(W/L)_{n,p}$  , decreases  $R_{on}$  but increases parasitic capacitors.

(4)

S/H Using Bootstrapped Circuit

a) With Ideal switches

# Circuit

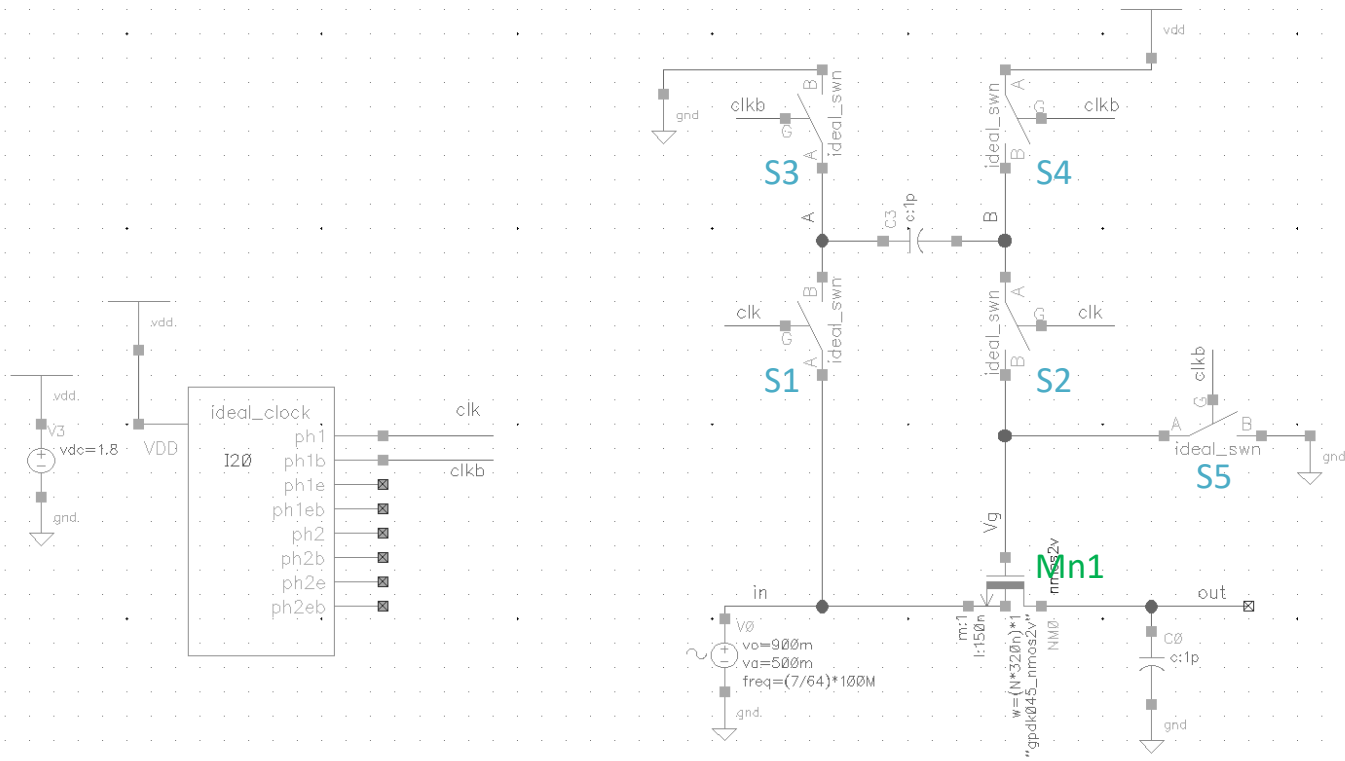

# Waveforms

Max size for best  
ENOB & performance

$$At \left( \frac{W}{L} \right)_{n1} = 34 \times \left( \frac{320nm}{150nm} \right)$$

Thu Mar 8 00:36:57 2018

Transient Response

Name V1c

clk

clk

Vin

Vg

Vg - Vin

Vg - Vin

A


B

A

B


Vout

Vout

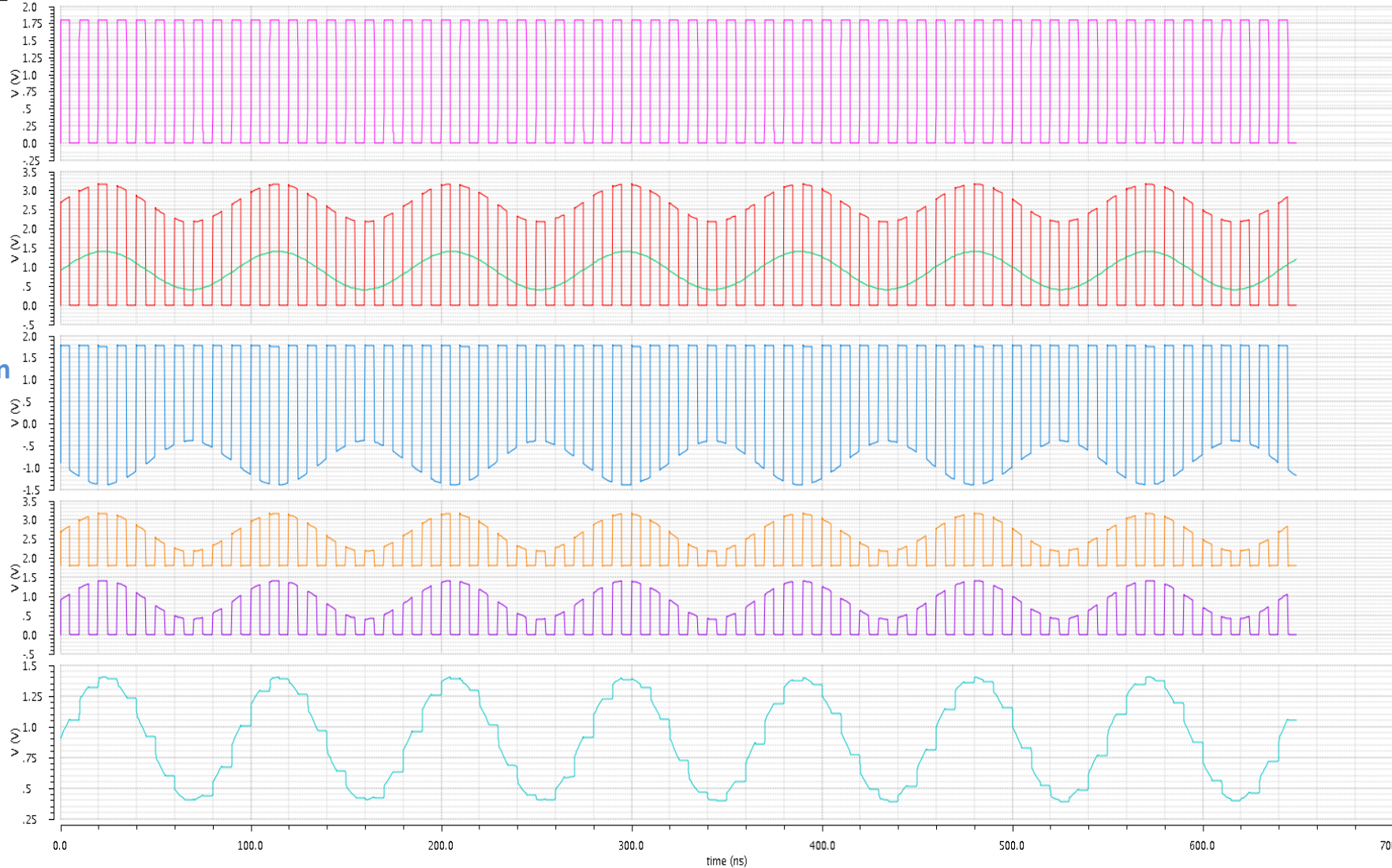

 
# DFT of output


db20(dft(v("out" ?result "tran") 9n 649.0n 64 "Rectangular"))



# DFT of output (MATLAB)

 

# Using PrettyFFT function

 

(4)

S/H Using Bootstrapped Circuit


b) Topology 1



[illegible]

Mohamed Dessouky and Andreas Kaiser, "Very Low-Voltage Digital-Audio  $\Delta\Sigma$  Modulator with 88-dB Dynamic Range Using Local Switch Bootstrapping", *IEEE J. Solid-State Circuits*, vol. 36, pp. 349–355, Mar. 2001

# Implemented Circuit

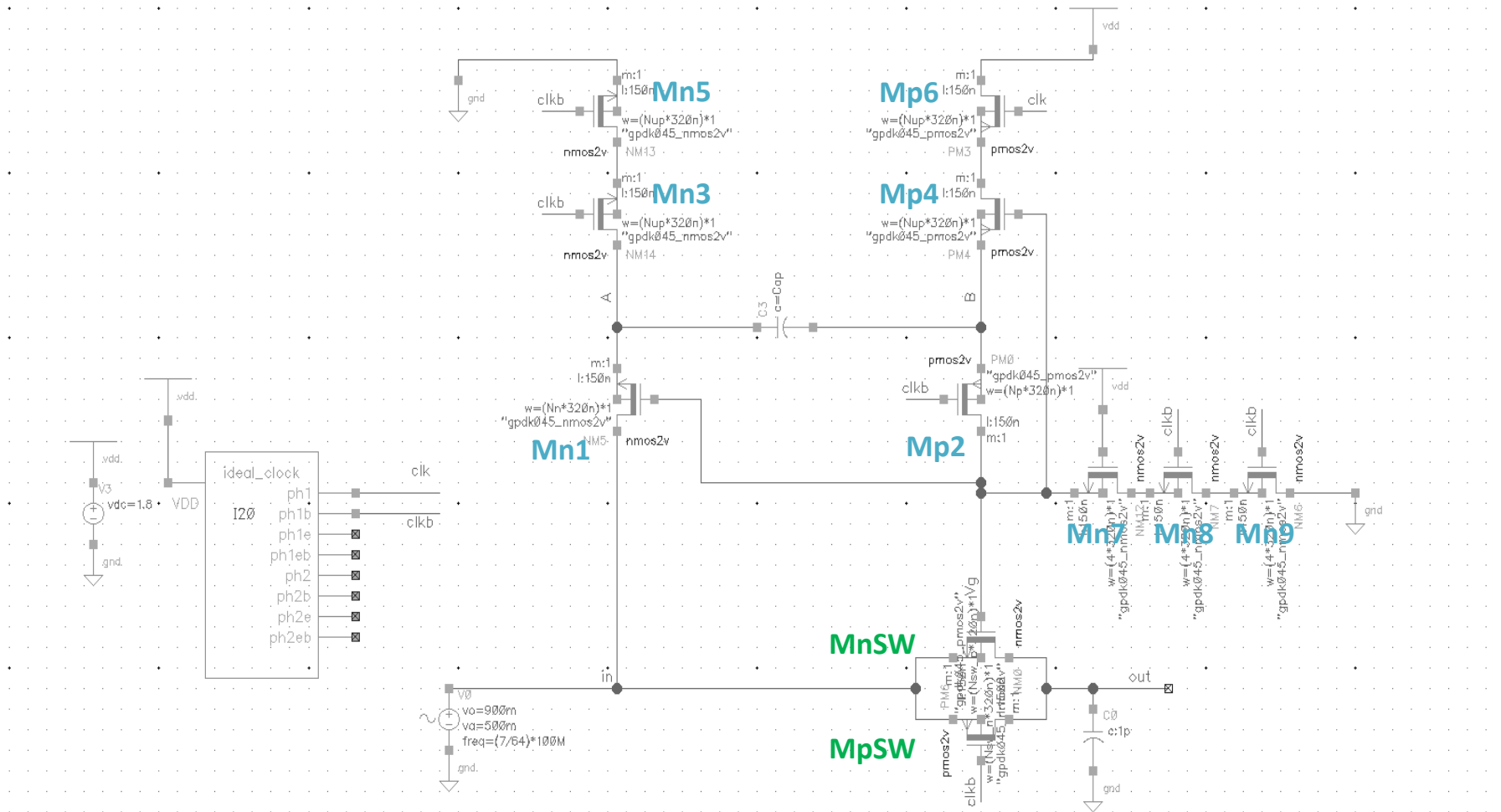

# Sizing & Modifications

1. **Mn3,Mp4** are added to decrease charge sharing, by separating nodes A & B of the offset Cap from the parasitic Cap of Mn5,Mp6 that are directly connected to the rails (when Mn5,Mp6 are off).
2. **Mn1,Mp6** have their gates connected to Vg node, since this node goes from gnd in clkb phase, to the highest potential in the circuit in clk phase. Thus causing Mn1,Mp6 to turn on & off much better.
3. **Mn8** is added to decrease charge sharing, by separating gate node Vg of MnSW from the parasitic Cap of Mn9 that is directly connected to gnd when Mn9 is off.
4. **MpSW** is added to assist MnSW when Vin is high & to decrease the equivalent resistance of the switch (the ENOB of the system increases from ~9.7 bits to ~10.6 bits).

→ Sizing:

Device	Size
MnSW	15 * (320n/150n)
MpSW	14 * (320n/150n)
Mn1	4 * (320n/150n)
Mp2	1 * (320n/150n)
Mn3,Mn5,Mp4,Mp6	1 * (320n/150n)
Mn7,Mn8,Mn9	4 * (320n/150n)
Offset Cap, Load Cap	1pF

# Waveforms

Transient Response

Thu Mar 8 01:10:06 2018

Name Vts

clk

clk


/in

Vin

Vg


/out

Vout

 

 
# DFT of output


db20(dft(v("out" ?result "tran") 9n 649.0n 64 "Rectangular"))



# DFT of output (MATLAB)

 

# Using PrettyFFT function

 

(4)


S/H Using Bootstrapped Circuit

c) Topology 2




# Original Circuit

## Nakagome Charge Pump

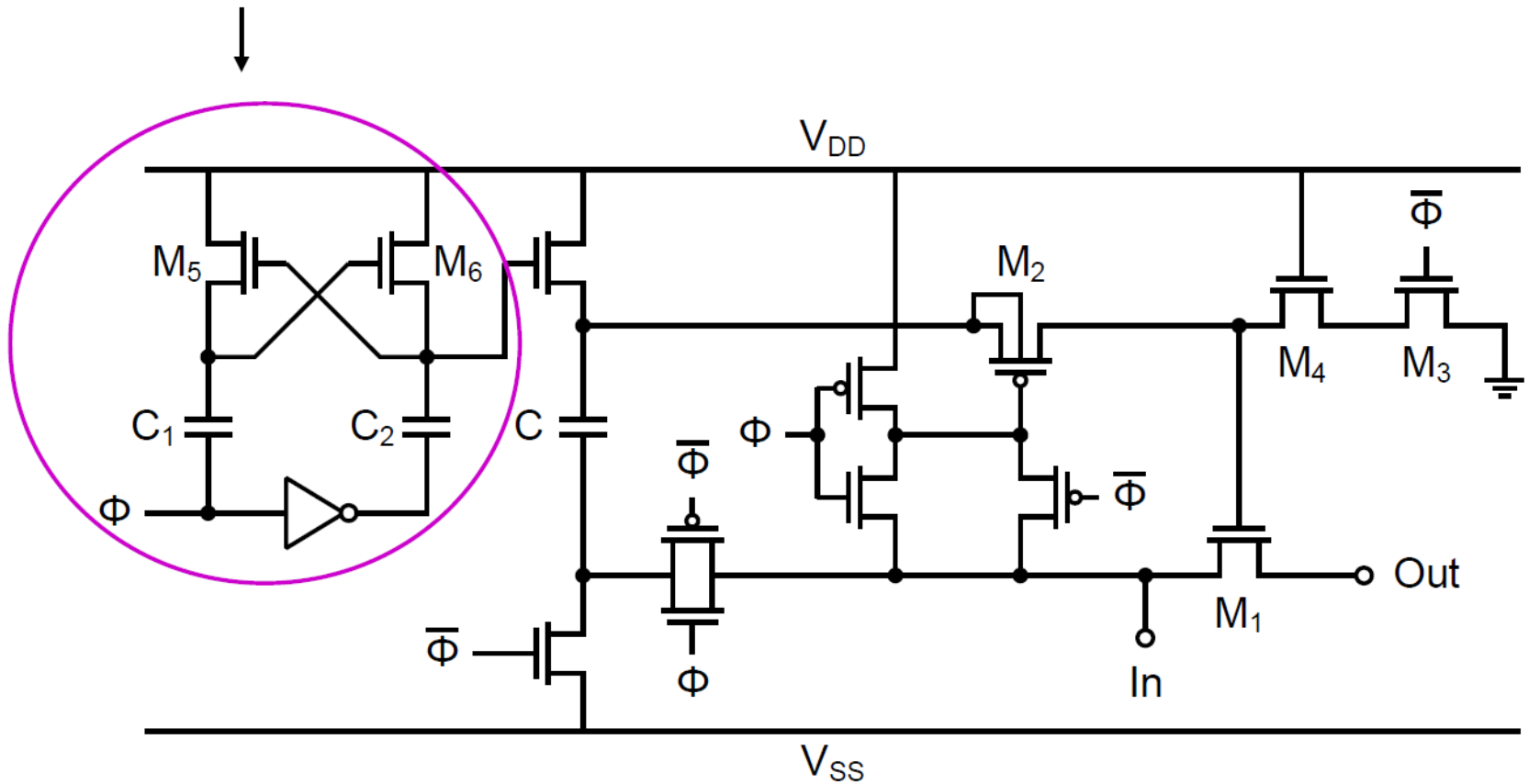

A. M. Abo and P. R. Gray, "A 1.5-V, 10-bit, 14.3-MS/s CMOS pipeline ADC", IEEE Journal of Solid-State Circuits, vol. 34, issue 5, pp. 599-606, 1999.

# Implemented Circuit

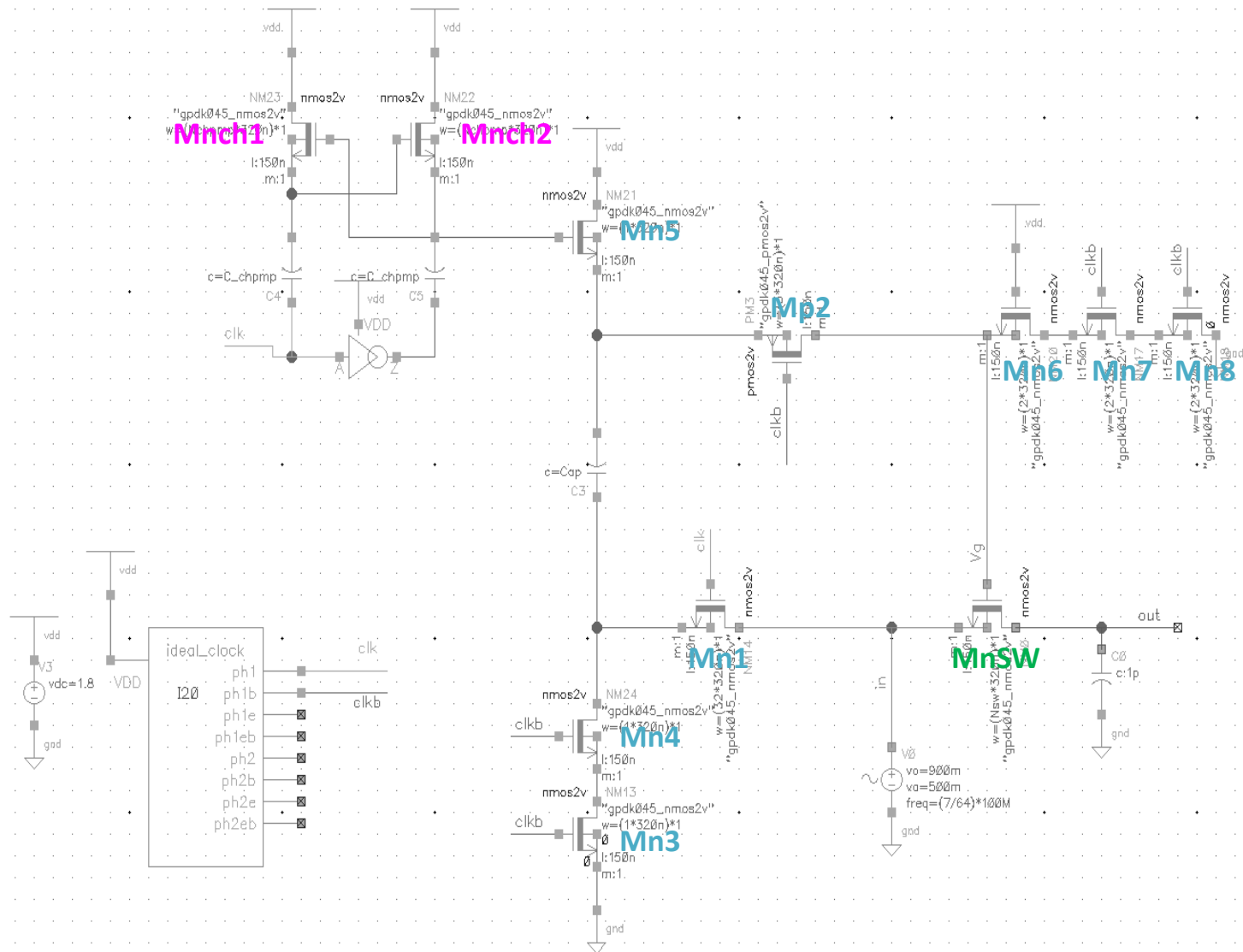

# Sizing & Modifications

1. **A Charge Pump** is connected to the gate of Mn5 to keep Vgs of Mn5 to be much greater than Vth, & have a switch that can pass a strong VDD signal.
2. **Mn4** is added to decrease charge sharing, by separating the offset Cap from the parasitic Cap of Mn3 that is directly connected to gnd when Mn3 is off.
3. **Mn7** is added to decrease charge sharing, by separating gate node Vg of MnSW from the parasitic Cap of Mn8 that is directly connected to gnd when Mn8 is off.

→ Sizing:

Device	Size
MnSW	<b>30</b> * (320n/150n)
Mnch1,Mnch2	<b>10</b> * (320n/150n)
Mn1	<b>32</b> * (320n/150n)
Mp2	<b>3</b> * (320n/150n)
Mn3,Mn4,Mn5	<b>1</b> * (320n/150n)
Mn6,Mn7,Mn8	<b>2</b> * (320n/150n)
Ch Pump Caps, Load Cap	<b>1pF</b>
Offset Cap	<b>4pF</b>

# Waveforms

Transient Response

Sat Mar 10 14:57:28 2018

Name Vis

clk

clk


Vin

Vin

Vg


Vout

Vout

 

 
# DFT of output


db20(dft(v("out" ?result: "tran") 9n 649.0n 64 "Rectangular"))



# DFT of output (MATLAB)

 

# Using PrettyFFT function

 

# SUMMARY

- For Full-Scale input = 1V, from 0.4V to 1.4V:

	Ideal	NMOS Only	PMOS Only	Transmission Gate	Bootstrap (with ideal switches)	Bootstrap (topology 1)	Bootstrap (topology 2)
ENOB	15.51 bits	3.37 bits	3.44 bits	9.29 bits	14.24 bits	<b>10.55 bits</b>	9.01 bits
SNR	95.12 dB	22.07 dB	22.49 dB	57.71 dB	87.51 dB	<b>65.27 dB</b>	55.99 dB
SFDR	102.85 dB	25.04 dB	25.35 dB	59.01 dB	88.35 dB	<b>67.00 dB</b>	56.78 dB

\* These are the best performances I was able to achieve for each case, after careful sizing of all the devices.



# SUMMARY

- For Full-Scale input = 0.5V, from 0.65V to 1.15V:

	Ideal	NMOS Only	PMOS Only	Transmission Gate	Bootstrap (with ideal switches)	Bootstrap (topology 1)	Bootstrap (topology 2)
ENOB	15.01 bits	6.62 bits	6.59 bits	8.20 bits	13.90 bits	<b>12.29 bits</b>	10.10 bits
SNR	92.13 dB	41.63 dB	41.29 dB	51.14 dB	85.43 dB	<b>75.76 dB</b>	62.56 dB
SFDR	96.36 dB	42.64 dB	42.91 dB	51.51 dB	88.84 dB	<b>77.95 dB</b>	63.27 dB

\* These results are achieved by only changing the input full-scale. The same sizes as before are used.

# SUMMARY

## Observations:

- The Bootstrapped techniques are shown to increase the ENOB, SNR, & SFDR, improving the performance.
- There is a tradeoff while sizing (W/L) of the transistors; Increasing (W/L), decreases the  $R_{on}$  of the transistors, but increases at the same time the parasitic capacitances of the transistors.
- The Matlab results show a greater noise floor level than that on Cadence in the cases where ideal switches were used.  
But the Matlab results are very close to that of Cadence in the NMOS/PMOS circuits & the Bootstrapped circuits.
- Decreasing the full-scale input, improves the circuit performance for all the cases, except the ideal circuits & the transmission gate circuit.